

PART - B

Test bench code

```
`timescale 1ns / 1ps

module tb_receiver;

    // Inputs
    reg clk;
    reg rst;
    reg rx;

    // Outputs
    wire [3:0] data;
    wire done;

    // Instantiate the receiver
    receiver uut (
        .clk(clk),
        .rst(rst),
        .rx(rx),
        .data(data),
        .done(done)
    );

    // Generate a clock: 10 ns period
    always begin
        #5 clk = ~clk;
    end

    // Task to send one 6-bit framed packet: start, 4 bits (LSB first), stop
    task send_packet(input [3:0] payload);
        integer i;
        begin
            @(posedge clk); #1 rx <= 0; // Start bit
            @(posedge clk); #1;

            for (i = 0; i < 4; i = i + 1) begin
                rx <= payload[i];
                @(posedge clk); #1;
            end

            rx <= 1; // Stop bit
            @(posedge clk); #1;
        end
    endtask
end
```

```
endtask
```

```
initial begin
```

```
    // Initial values
```

```
    clk = 0;
```

```
    rst = 1;
```

```
    rx = 1;
```

```
    // Hold reset for 2 cycles
```

```
    repeat (2) @(posedge clk);
```

```
    rst <= 0;
```

```
    // Send valid packet: 4'b1010
```

```
    send_packet(4'b1010);
```

```
    // Idle for 4 cycles
```

```
    repeat (4) @(posedge clk);
```

```
    // Send valid packet: 4'b0111
```

```
    send_packet(4'b0111);
```

```
    // Idle for 4 cycles
```

```
    repeat (4) @(posedge clk);
```

```
    // Send invalid packet (bad stop bit)
```

```
    @(posedge clk); #1 rx <= 0; // Start bit
```

```
    @(posedge clk); #1 rx <= 1;
```

```
    @(posedge clk); #1 rx <= 0;
```

```
    @(posedge clk); #1 rx <= 1;
```

```
    @(posedge clk); #1 rx <= 1;
```

```
    @(posedge clk); #1 rx <= 0; // Incorrect stop bit
```

```
    // Let it sit idle for recovery
```

```
    repeat (6) @(posedge clk); #1;
```

```
    rx <= 1;
```

```
    // Send one more valid packet: 4'b1100
```

```
    repeat (2) @(posedge clk);
```

```
    send_packet(4'b1100);
```

```
    // End simulation
```

```
    repeat (10) @(posedge clk);
```

```
    $finish;
```

```
end
```

```
// Dump waveform for viewing in GTKWave or similar
```

```
initial begin
```

```
    $dumpfile("receiver.vcd");
```

```
    $dumpvars(0, tb_receiver);  
end
```

```
endmodule
```

VERILOG CODE

```
module receiver (  
    input clk,  
    input rst,  
    input rx,          // Serial bitstream input  
    output reg [3:0] data, // Received 4-bit data  
    output reg done     // Done pulse when valid byte received  
);
```

```
    // Counter for 4 data bits  
    reg [2:0] bit_cnt;  
    reg [3:0] shift_reg;
```

```
    // Define FSM states using SystemVerilog enum  
    typedef enum reg [2:0] {  
        IDLE      = 3'd0,  
        RECEIVE   = 3'd1,  
        WAIT_STOP = 3'd2,  
        DONE      = 3'd3,  
        ERROR     = 3'd4  
    } state_t;
```

```
    state_t state, next_state;
```

```
    // Sequential block for state, output, and data  
    always @(posedge clk or posedge rst) begin
```

```
        if (rst) begin  
            state    <= IDLE;  
            bit_cnt  <= 3'd0;  
            shift_reg <= 4'd0;  
            data     <= 4'd0;  
            done     <= 1'b0;  
        end else begin  
            state <= next_state;
```

```
        case (state)  
            IDLE: begin  
                done <= 1'b0;  
                if (rx == 1'b0) begin // Start bit detected  
                    bit_cnt  <= 3'd0;  
                    shift_reg <= 4'd0;  
                end  
            end  
        end
```

```
        RECEIVE: begin
```

```

        shift_reg <= {rx, shift_reg[3:1]}; // Shift in new bit
        bit_cnt <= bit_cnt + 1;
    end

    WAIT_STOP: begin
        if (rx == 1'b1) begin // Valid stop bit
            data <= shift_reg;
            done <= 1'b1;
        end
    end

    DONE: begin
        done <= 1'b0; // Pulse done signal
    end

    ERROR: begin
        done <= 1'b0; // Wait for idle line
    end
endcase
end
end

// Combinational next-state logic
always @(*) begin
    next_state = state;
    case (state)
        IDLE:
            next_state = (rx == 1'b0) ? RECEIVE : IDLE;

        RECEIVE:
            next_state = (bit_cnt == 3'd3) ? WAIT_STOP : RECEIVE;

        WAIT_STOP:
            next_state = (rx == 1'b1) ? DONE : ERROR;


        DONE:
            next_state = IDLE;

        ERROR:
            next_state = (rx == 1'b1) ? IDLE : ERROR;
    endcase
end

endmodule

```

STATE DIAGRAM:

 

This is a Verilog implementation of a serial bit receiver using a finite state machine (FSM). The design follows a standard framed format where each valid transmission consists of a start bit (**0**), followed by 4 data bits, and ends with a stop bit (**1**). The line remains at logic high (**1**) when idle.

The FSM has the following states:

- **IDLE**: waits for the start bit
- **RECEIVE**: collects 4 bits one by one
- **WAIT_STOP**: checks for the stop bit
- **DONE**: indicates the data is valid and received
- **ERROR**: entered if the stop bit is invalid

The FSM uses a **state** and **next_state** approach. The current state is updated every clock cycle, and transitions are determined based on inputs. The output **done** is asserted only in the **DONE** state, making it a Moore FSM.

When in **IDLE**, if a **0** is detected on **rx**, it moves to **RECEIVE**. During the **RECEIVE** state, a 4-bit shift register stores incoming bits. After 4 bits, it expects a stop bit. If the

stop bit is correct (`rx == 1`), it transitions to **DONE** and outputs `done = 1` for one cycle. If the stop bit is not 1, it goes to **ERROR**, where it waits until the line goes idle again before returning to **IDLE**.

This type of FSM can be used in low-level serial data handling systems like UART or other custom serial protocols. The design uses `typedef enum` for defining state values and ensures stable transitions with synchronous reset and proper error recovery.

This receiver can be further extended with parity checking, wider data frames, or buffering using a FIFO for continuous reception.